

Design of control unit

→ A control unit - generates a set of signals that are in syn with the master clock.

→ Two major operations perform by control unit are:-

① To fetch the data from the main memory, determines the device and the operations involved with it.

② Produce control signals to execute the operations.

Types of control unit


① Hardwired control

② Microprogrammed control

① Hardwired control

This organization involves the control logic to be implemented with gates, flipflops, decoders, and other digital circuits.

Instruction Register (IR)

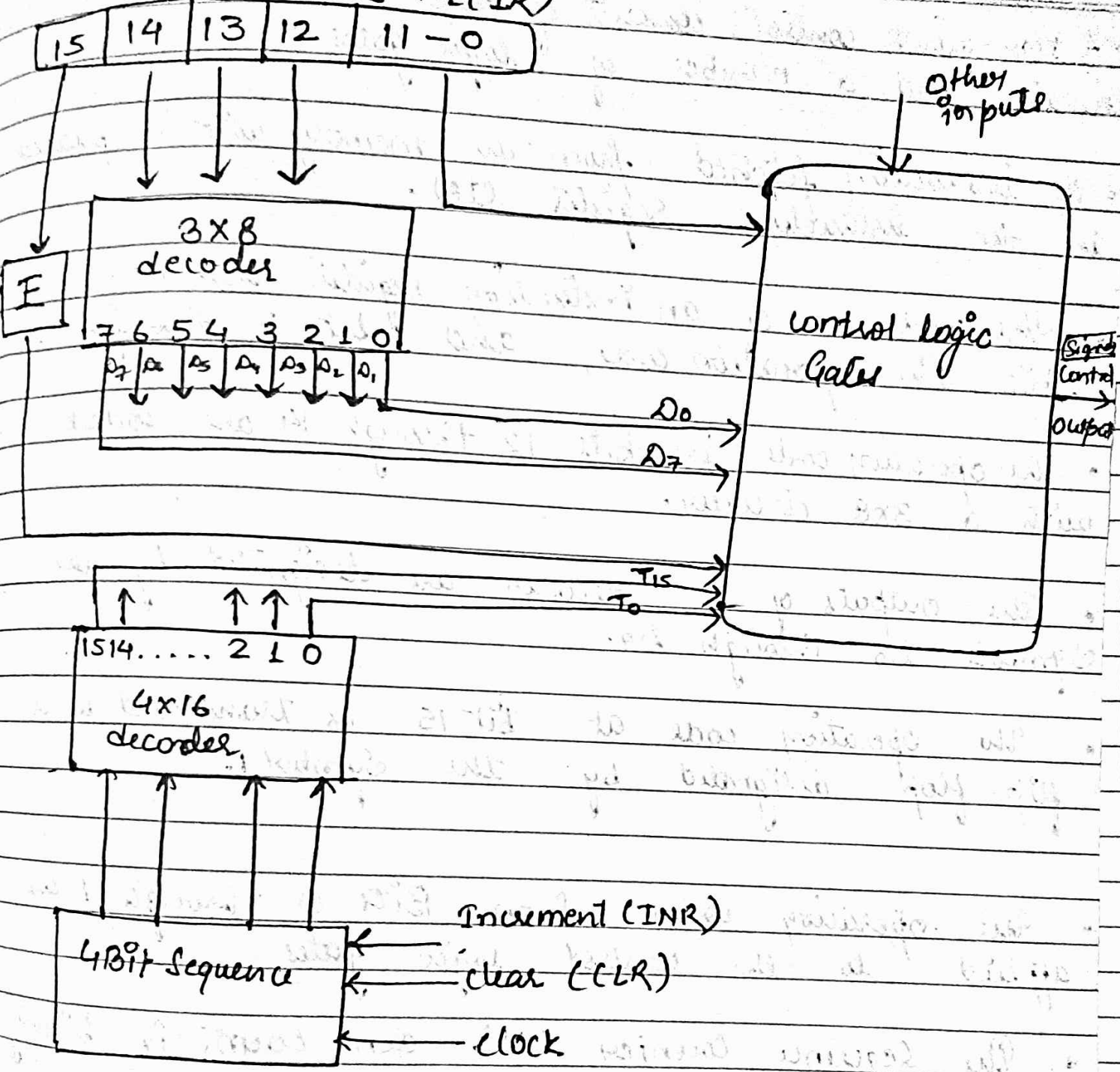

• A Hardwired control consists of two decoders, a sequence counter, and a number of logic gates.

• An instruction fetched from the memory unit is placed in the instruction register (IR).

• The component of an instruction register includes, 1 bit, the operation code, and bits 0 through 11.

• The operation code in bits 12 through 14 are coded with a 3x8 decoder.

• The outputs of the decoder are designated by the symbols D0 through D7.

• The operation code at bit 15 is transferred to a flip-flop designated by the symbol 1.

• The operation codes from Bits 0 through 11 are applied to the control logic gates.

• The sequence counter (SC) can count in binary from 0 through 15.